

6.09)

$$V_{DD} = 1.8V \quad \frac{W}{L} = 20 \quad V_{Th} = 0.4V \quad N_mC_{ox} = 200 \frac{nA}{V^2}$$


$$R_{on} = \frac{1}{N_mC_{ox} \frac{W}{L} (V_{DD} - V_{Th})} = \frac{1}{\left(200 \frac{nA}{V^2}\right) \left(20\right) (1.8 - 0.4)V} = 179 \Omega$$

6.12)

$$R_{on} = \frac{1}{N_mC_{ox} \frac{W}{L} (V_{GS} - V_{Th})} \Rightarrow T = R_{on} C_{GS} = \frac{W_mC_{ox}}{N_mC_{ox} \frac{W}{L} (V_{GS} - V_{Th})} = \frac{L^2}{N(V_{GS} - V_{Th})}$$

Para manter a constante de tempo, use o comprimento mínimo de um canal e mantenha a tensão sobreposta.

6.14)

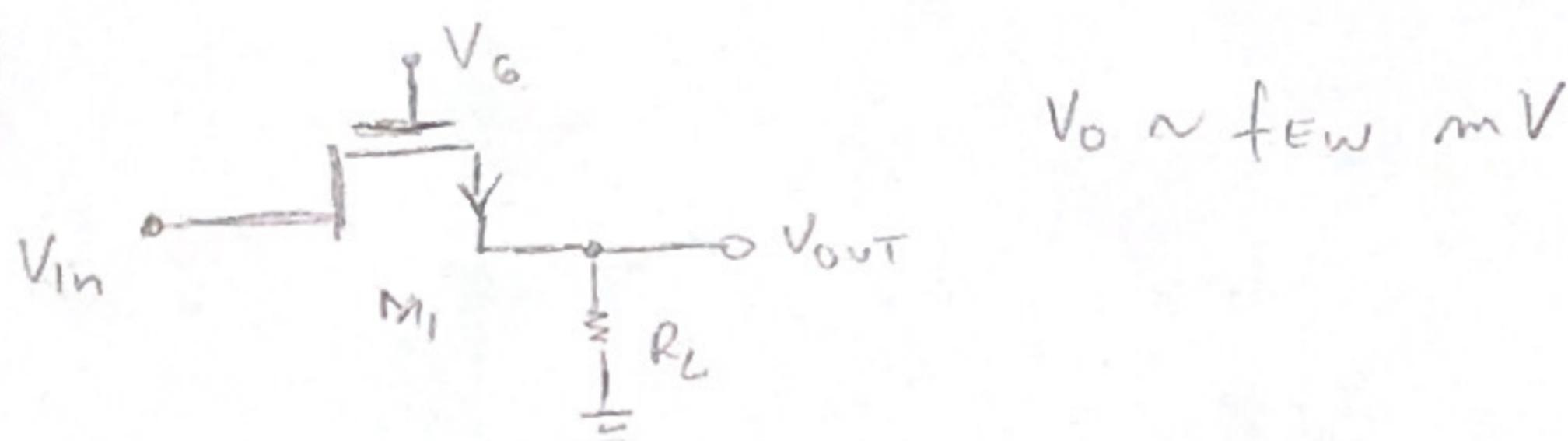

$$V_o \approx \text{few mV}$$

$$(a) \quad V_{in} = V_0 \cos \omega t \quad V_{out} = 0.95 (V_0 \cos \omega t)$$

$$V_{out} = \frac{R_L}{R_{on} + R_L} \cdot V_{in} \Rightarrow \frac{R_L}{R_{on} + R_L} = 0.95$$

$$R_{on} = \frac{R_L}{\frac{0.95V_0}{1 - 0.95V_0}} = \frac{1}{N_mC_{ox} \frac{W}{L} (V_0 - V_{Th})} \Rightarrow \frac{W}{L} = \frac{0.95V_0 / (1 - 0.95V_0)}{N_mC_{ox} R_L (V_0 - V_{Th})}$$

$$(b) \quad V_{out} = 0.95 V_{in} = 0.95 (V_{in} + 0.5) \approx 0.95 \times 0.5 = 0.475$$

$\Rightarrow V_0$ é muito pequena.

$$R_{on} = \frac{R_L}{0.9} = \frac{1}{N_mC_{ox} \frac{W}{L} (V_0 - V_{Th})} \Rightarrow \frac{W}{L} = \frac{0.9}{N_mC_{ox} R_L (V_0 - V_{Th})}$$

6.24)

$$V_{DD} = 1.8V \quad \lambda = 0$$


$$V_{DS} \geq V_{GS} - V_{Th}$$

$$\Rightarrow V_{GS} \geq 1 - 0.4 = 0.6V$$





$$\Rightarrow \frac{1}{2} N_mC_{ox} \frac{W}{L} (V_{GS} - V_{Th})^2$$

$$= \frac{1}{2} \left(200 \frac{nA}{V^2}\right) \left(\frac{10}{0.18}\right) (0.6)^2 = 2mA$$

$$\frac{V_{DD} - V_{DS}}{R_D} = 2mA$$

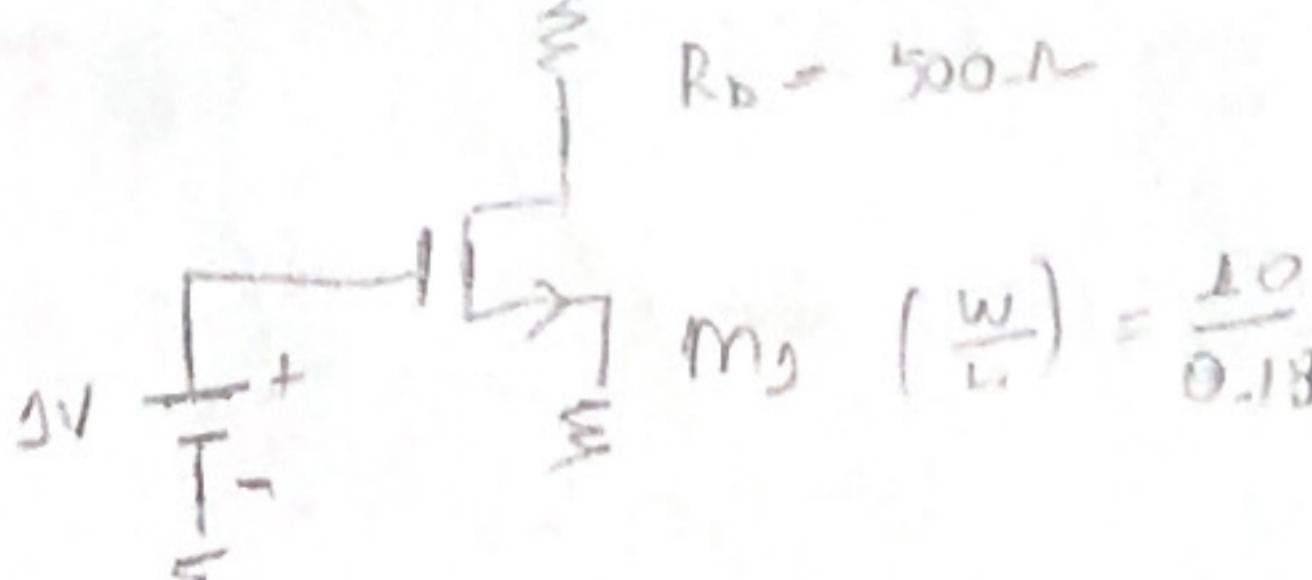

6.28)

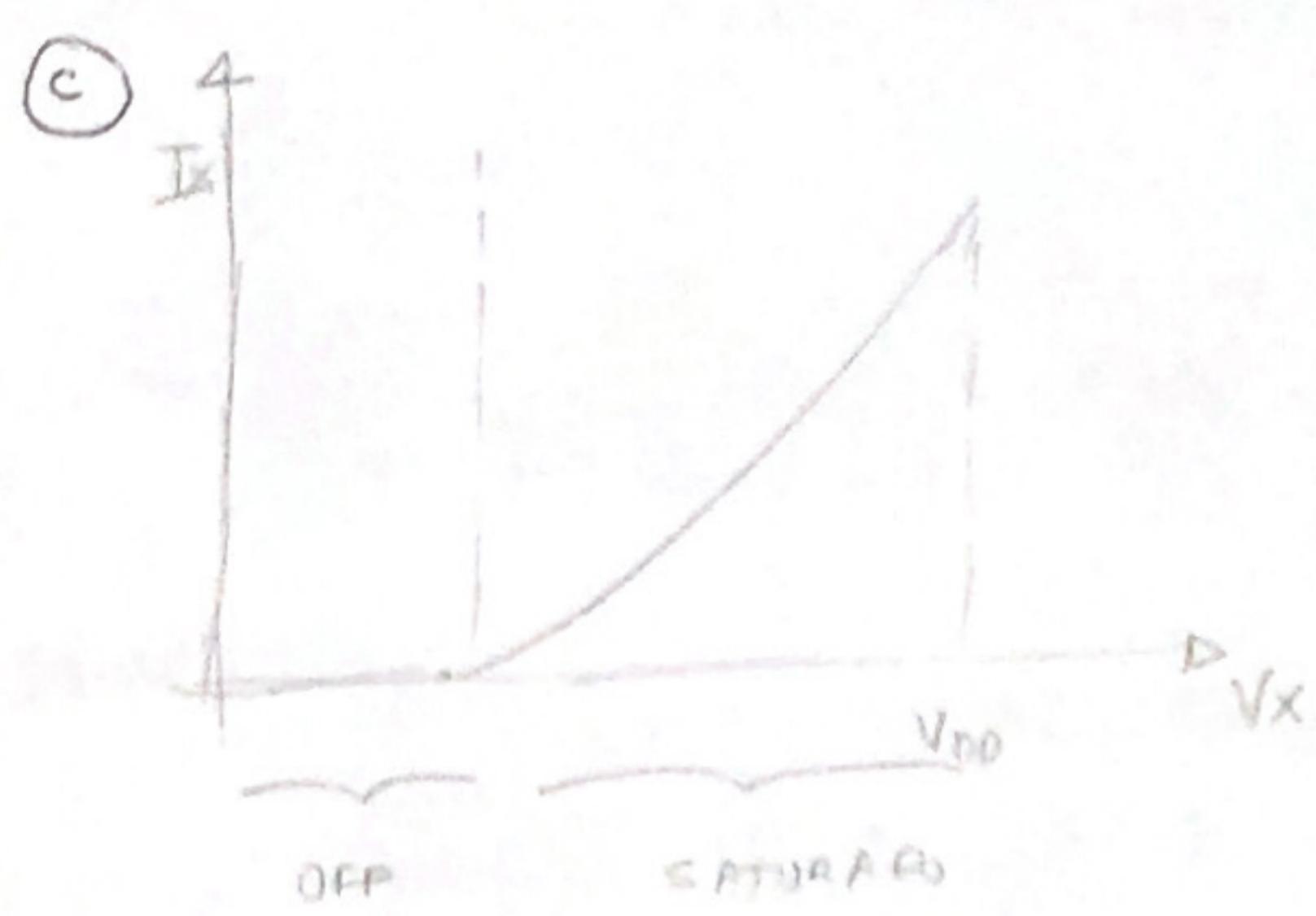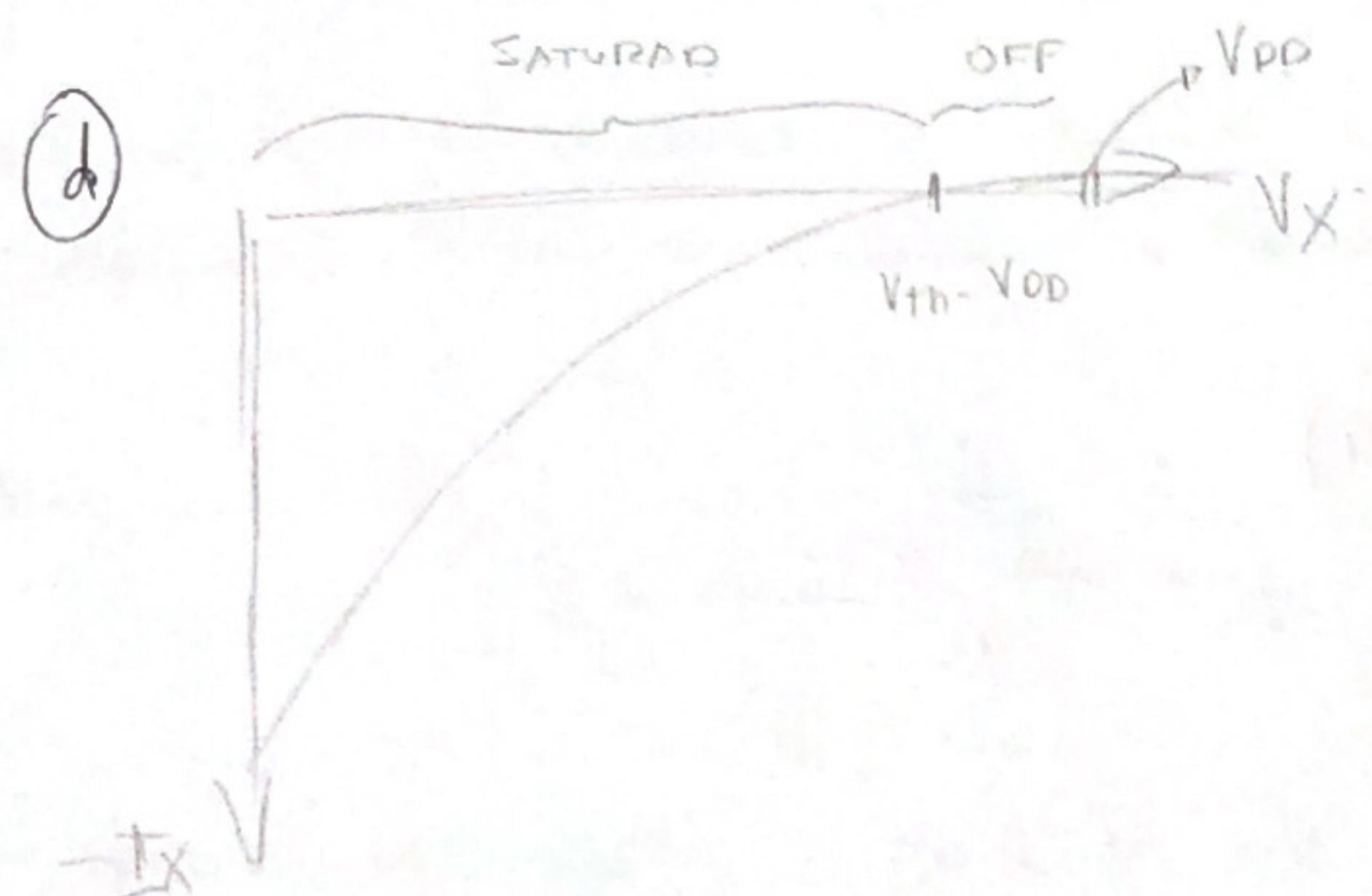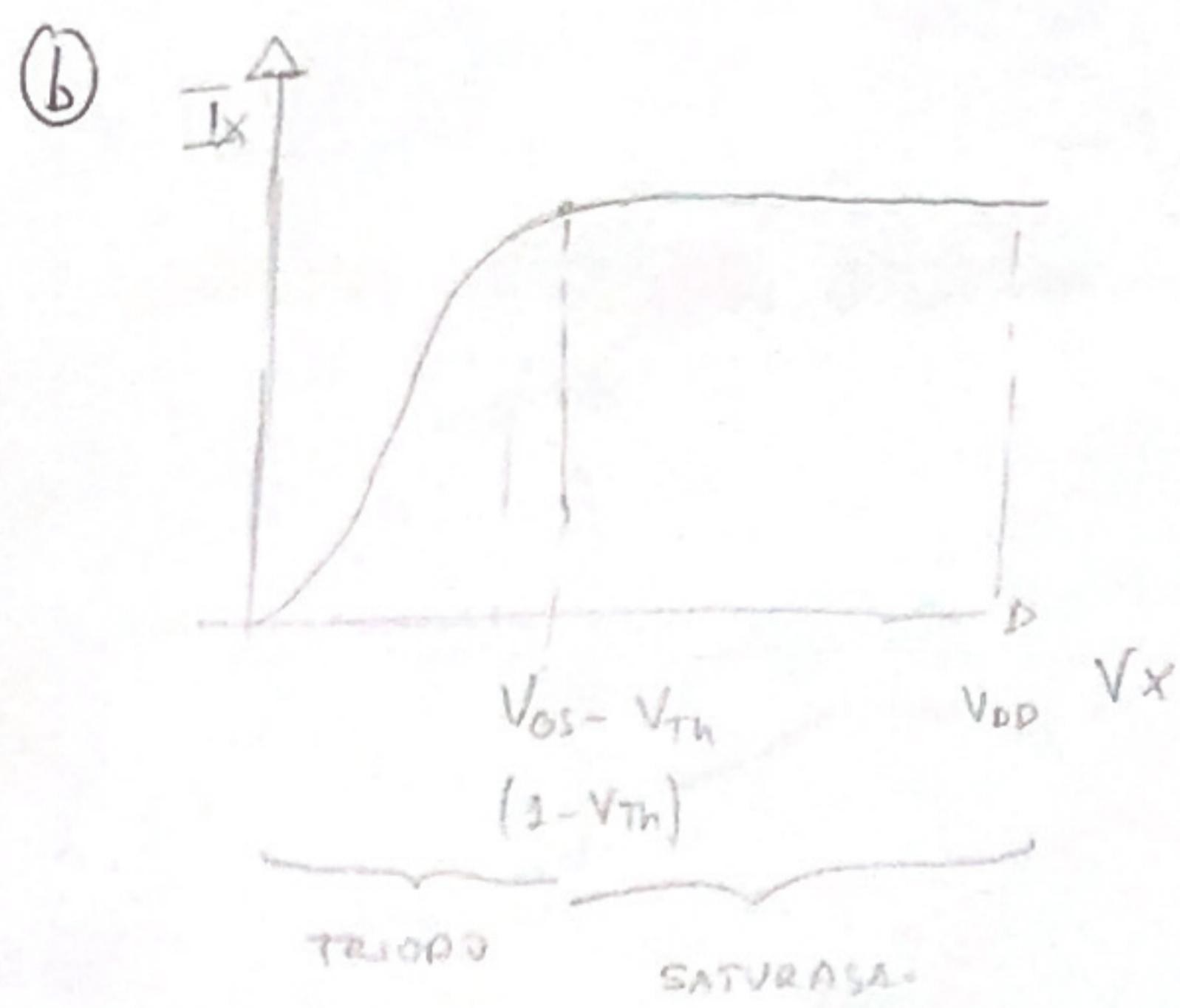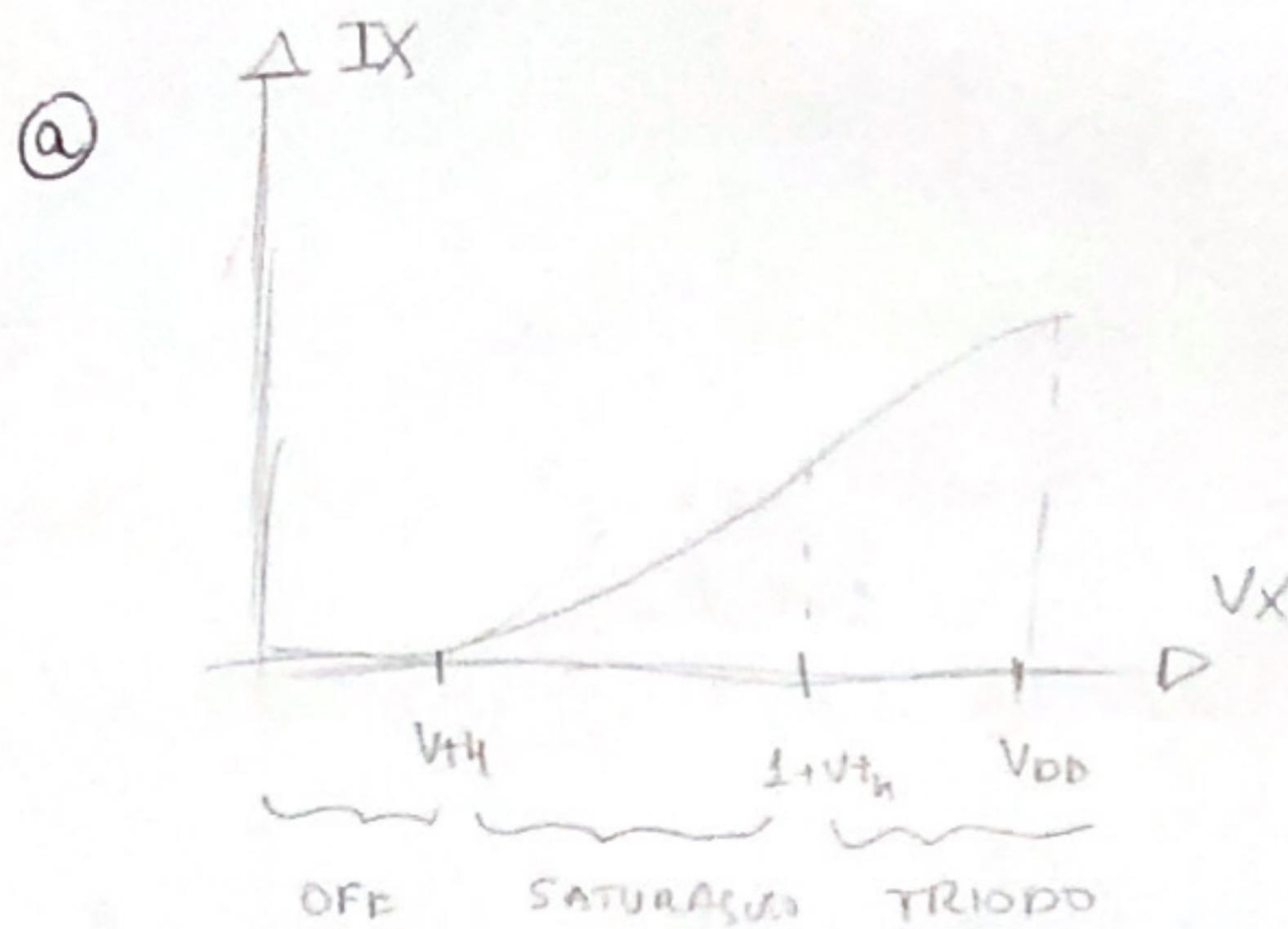

6.33) a) $V_{DS} = V_{DD} - I_D R_D = V_{DD} - R_D \cdot \frac{1}{2} \mu n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) (1 + 2V_{DS})$

$$= 18 - 100 \cdot \frac{1}{2} \cdot 200 \left(\frac{20}{0.1} \right) (1 - 0.4)^2 (1 + 2V_{DS}) \Rightarrow V_{DS} = 1.35V$$

$$V_{DS} > V_{GS} - V_{th} \quad g_m = \mu n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) = \left(200 \right) \left(\frac{20}{0.1} \right) \left(1 - 0.4 \right) \\ = 0.013 \text{ A/m}$$

$$R_D = \frac{1}{\lambda I_D} = \frac{1}{\lambda \left(\frac{V_{DD} - V_{DS}}{R_D} \right)} = \frac{1}{0.2 \left(\frac{0.65}{100} \right)} = 2222 \Omega$$

7.17)

$$a) I_{D1} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{5}{0.19} \right) (V_B - 0.4)^2 = (2 + 0.1 \times 0.8) \Rightarrow V_B = 0.806 V$$

b) há 3 regimes de operação


- $V_X < V_B - V_{TH}$ (modo | $I_{DS2}| > |I_{DS1}|$)

- $|V_X - V_{DD}| > |V_B - V_D - V_{TH}|$ (modo $|I_{DS1}| > |I_{DS2}|$)

- $V_B - V_{TH} < V_X < |V_X - V_{DD}| < |V_B - V_D - V_{TH}|$

$M_1 \rightarrow M_2$ em saída e $|I_{S1}| = |I_{DS2}| = 0.5 \text{ mA}$ $V_K = 0.3 V$

Também $I_{DS1} = I_{DS2} = I_{DS}$

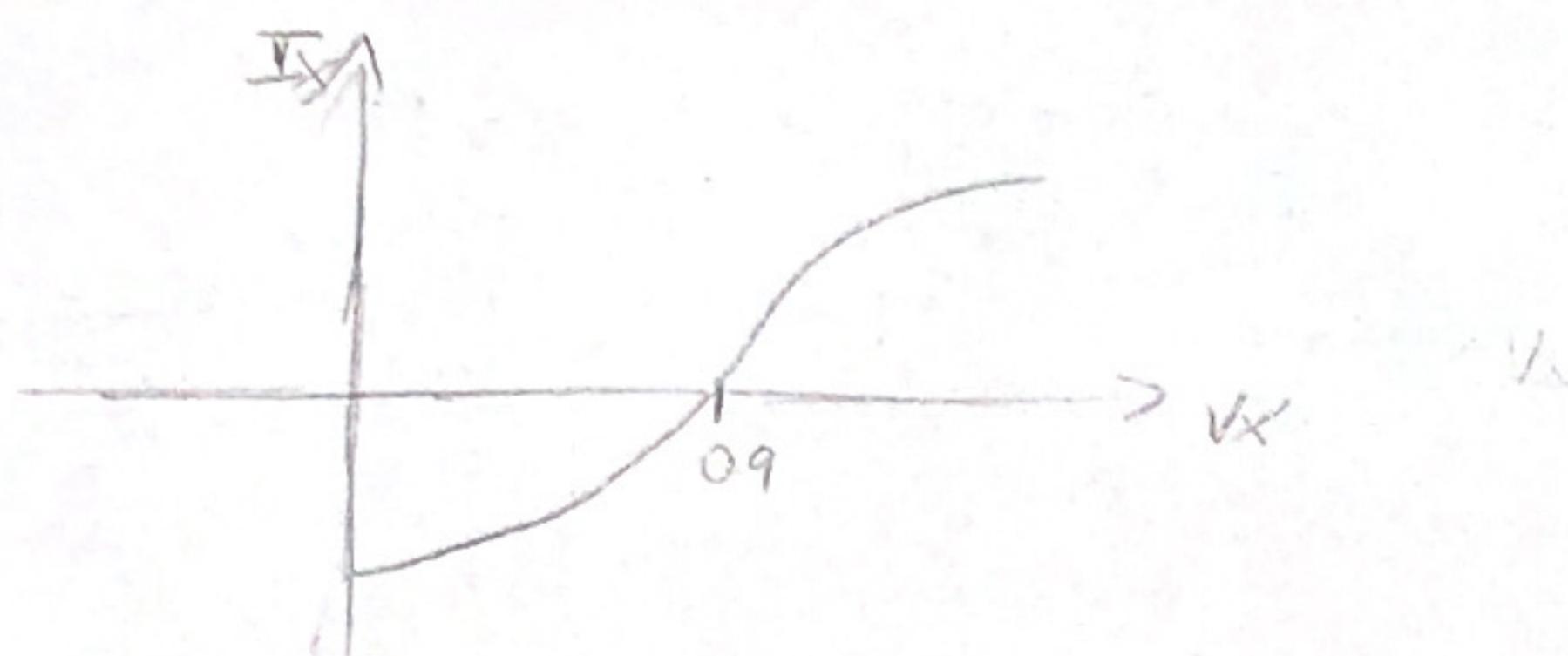

7.19) $(A_v) = 5 \rightarrow P(w) = I_{DS} \times V_{DD} \quad P \leq 1 \text{ mW} \quad I_{DS} / 18 \leq 1 \text{ mV}$

$f_m R_o = 5 \quad I_{DS} \leq 0.556 \text{ mA} \quad f_m = \sqrt{2 A_{fes}}$

$$f_{m\max} = \sqrt{2 \times 200 \times 10^{-6} \times \left(\frac{5}{0.19} \right)} \times 0.55 \text{ mA} = 2.00487 \text{ Hz} \quad R_o = \frac{5}{0.00487} = 10.06 \Omega$$

15.25) Consider os circuitos a) b) c) respectivamente.

Consider os graficos 1) 2) 3) respectivamente

a) $\rightarrow 1)$ b) $\rightarrow 3)$ c) $\rightarrow 2)$

15.26) $R_o = 2k \quad \left(\frac{w}{l} \right)_1 = 3/0.19 \quad \left(\frac{w}{l} \right)_2 = 5/0.19 \quad V_{DD}, V_{OH}, V_{MTRD} = ?$

$$I_{DS} = \frac{1}{2} N_D \log \left(\frac{w}{l} \right)_2 \left[2(V_{DD} - V_{TH2})(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$\frac{V_{out}}{R_o} = \frac{1}{2} N_D C_{ox} \left(\frac{w}{l} \right)_2 \left[2(V_{DD} - V_{TH2})(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$V_{out} = 0.25 V_{out} - 1 \text{ mV} = 0 \quad V_{out} - V_{out} = 1.348 V$$

$$① V_{in} = V_{out}$$

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p} \quad \frac{1}{2} N_a C_{ox} \left(\frac{W}{L} \right)_2 \left(V_{DD} - V_{in} + |V_{TH2}| \right)^2 =$$
$$\frac{1}{2} N_a C_{ox} \left(\frac{W}{L} \right)_2 \left(V_{in} - V_{TH} \right)^2 + \frac{V_{out}}{2 \alpha}$$

$$0.05 V_{out}^2 + 0.59 V_{out} - 0.3945 = 0 \rightarrow V_{in} = V_{out} = 0.6V$$